

Digital Electronics Interview Questions and Answers – (Updated 2020)



admin

11 months ago

Digital Electronics Interview Questions



BYJU'S



If you are looking for a job which is related to Digital Electronics then you need to prepare for **Digital Electronics Interview Questions**. Here, we have prepared important Digital Electronics Interview Questions and Answers which will help you get success in your Interview. Check Updated Digital Electronics Interview Questions 2020 from here.

recruitmentresult.com



BYJU'S

Comprehensive Study Material.

INSTALL




Digital Electronics Interview Questions

It is true that every interview is different as per different job profiles. These Digital Electronics Interview Questions are divided into two parts: Part 1 – Digital Electronics Interview Questions (Basic) & Part 2 – Digital Electronics Interview Questions (Advanced).

Digital Electronics Interview Questions with Solutions:

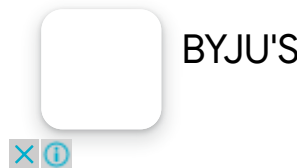Part 1: Digital Electronics Interview Questions (Basic):




Fresher candidates must go through these below given Digital Electronics Interview Questions that will help you to clear the Digital Electronics Questions with Answers PDF for Interview.

Ques1: What is the difference between D-latch And D Flip-flop?

Ans: D-latch is level sensitive where as a flip-flop is edge sensitive. Flip-flops are made up of latches.

Must Read Latest: [Interview Questions and Answers](#)

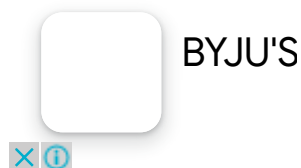

Ques2: What Is A Multiplexer?

Ans: Is a combinational circuit that selects binary information from one of many input lines and directs it to a single output line. ($2n \Rightarrow n$), where n is selection line.

Ques3: How Can You Convert The Jk Flip-flop To A D Flip-flop?



Install

Kormo Jobs by Google: Find
4.2 FREE

Ans: By connecting the J input to the K through the inverter.

Ques4: How Do You Detect If Two 8-bit Signals Are Same?

Ans: XOR each bits of A with B (for e.g. A [0] xor B [0]) and so on. The o/p of 8 XOR gates is then given as i/p to an 8-i/p nor gate. if o/p is 1 then A=B.

Part 2 – Digital Electronics Interview Questions (Advanced)

Ques5: What Is Race-around Problem? How Can You Rectify It?

Ans: The clock pulse that remains in the 1 state while both J and K are equal to 1 will cause the output to complement again and repeat complementing until the pulse goes back to 0, this is called the race around problem. To avoid this undesirable operation, the clock pulse

must have a time duration that is shorter than the propagation delay time of the F-F, this is restrictive so the alternative is master-slave or edge-triggered construction.

Also Read: [Interview Preparation Tips](#)

Ques6: How Will You Implement A Full Subtractor From A Full Adder?

Ans: All the bits of subtrahend should be connected to the xor gate. Other input to the xor being one. The input carry bit to the full adder should be made 1. Then the full adder works like a full subtract.

Ques7: In A 3-bit Johnson's Counter What Are The Unused States?

Ans: $2^n - 2$ is the one used to find the unused states in Johnson counter. So for a 3-bit counter it is $8 - 6 = 2$. Unused states = 2. the two unused states are 010 and 101.

Ques8: What Is Difference Between Ram And Fifo?

Ans: FIFO does not have address lines. Ram is used for storage purpose where as FIFO is used for synchronization purpose i.e. when two peripherals are working in different clock domains then we will go for FIFO.

Ques9: Is It Possible To Reduce Clock Skew To Zero? Explain Your Answer?

Ans: Even though there are clock layout strategies (H-tree) that can in theory reduce clock skew to zero by having the same path length from each flip-flop from the pll, process variations in R and C across the chip will cause clock skew as well as a pure H-Tree scheme is not practical (consumes too much area).

Do You Know: [Best Tips to Prepare for a Job Interview](#)

Ques10: How many types of number system are there?

Ans: There are four types of number system:

1. Decimal Number System.
2. Binary Number System.
3. Octal Number System.
4. Hexadecimal Number System.

Digital Electronics Interview Questions (Basic / Advanced)

Ques11: What is a Logic gate?

Ans: The basic gates that make up the digital system are called a logic gate. The circuit that can operate on many binary inputs to perform a particular logic function is called an electronic circuit.

Ques12: What is meant by K-Map or Karnaugh Map?

Ans: K-Map is a pictorial representation of truth table in which the map is made up of cells, and each term in this represents the min term or max term of the function. By this method, we can directly minimize the Boolean function without following various steps.

Ques13: Name the two forms of Boolean expression?

Ans: The two forms of Boolean expression are:

1. Sum of products (SOP) form.
2. The Product of sum (POS) form.

Must Know: [Common Interview Mistakes](#)

Ques14: What are the limitations of the Karnaugh Map?

Ans: The limitations of Karnaugh Map are as follows:

1. It is limited to six variable maps which means more than six variable involving expressions are not reduced.
2. These are useful for only simplifying Boolean expression which is represented in standard form.

Ques15: What are the applications of Multiplexer (MUX)?

Ans: The applications of the multiplexer are as follows:

1. It is used as a data selector from many inputs to get one output.
2. It is used as A/D to D/A Converter.
3. These are used in the data acquisition system.
4. These are used in time multiplexing system.

Ques16: What is Electronic?

Ans: The study and use of electrical devices that operate by controlling the flow of electrons or other electrically charged particles

Ques17: What is sampling?

Ans: The process of obtaining a set of samples from a continuous function of time $x(t)$ is referred to as sampling.

Must Read: [Interview Tips for Freshers](#)

Ques18: Why is Digital Electronics important?

- All real life signals are analog in nature and at first sight; it seems use of analog is much better as compared to digital signal.
- Digital signal is used in communication process to minimize the effect of noise.

Ques19: Who invented digital electronics?

Ans: The Z3 was an electromechanical computer designed by Konrad Zuse.

Ques20: What are digital techniques?

- Digital electronics or digital (electronic) circuits are electronics that operate on digital signals
- Digital techniques are helpful because it is a lot easier to get an electronic device

Digital Electronics Interview Questions and Answers (Updated 2020):

Before appearing for the Interview, you must completely revise all that you have studied about Digital electronics during your Graduation and Post-Graduation. By doing so, you will be able to clear all your doubts and confusion. Also, you must read all the Digital Electronics Interview Questions to increase your knowledge as the interview can be quite tricky.

Candidates May Also Search For:

- Digital Electronics Interview Questions for VLSI
- Digital Electronics Interview Questions Asked in TCS
- Digital Electronics Tricky Questions
- Digital Electronics Tough Questions

- [Digital Electronics Question Bank with Answers PDF](#)
- [Digital Electronics Questions And Answers PDF](#)
- [Digital Electronics Interview Questions MCQ](#)
- [Digital Electronics Interview Questions And Answers PDF Free Download](#)
- [Digital Electronics Interview Questions And Answer for Freshers PDF](#)

By going through these Digital Electronics Interview Questions, you will be able to appear in the interview with full confidence and can easily answer any question asked in Interview. This will ensure your selection for the Digital Electronic jobs. You can also get Digital Electronics Interview Questions and Answers PDF from here.

[Something That You Should Put An Eye On](#)

Sarkari Naukari	Latest Jobs By Qualification
Latest Private Jobs	Latest Recruitments
What Are Your Strength & Weakness?	Difference Between Resume And CV
Interview Tips for getting Job	Why Should We Hire You

Categories: [Interview](#), [Question & Answers](#)

Tags: [updates](#)

[Leave a Comment](#)

Recruitment result 2021

[Back to top](#)