

Modulation, demodulation, sampling, sampling

Types of modulation

Communication

CW modulation, Audio modulation

AM & FM, RF

PAM, PDM, PPM, PCM

Techniques of analog & digital

Diode, transistor, IC,

Resistor, Conductor, Inductor, semiconductor

Amplifier, Oscillator, repeater, rheostat, +ve & -ve & 1/B

Advantages of resistor

Cutoff freq, pass band, stop band, base material

Feedback, types $\begin{cases} +ve \\ -ve \\ bipolar \end{cases}$

Handover
Cross talk
Bluetooth

CDMA
TDMA
FDMA

OP-amp
instrumentational amplifier

Capacitor, rectifier

DIGITAL ELECTRONICS

1) Number system

Decimal (with decimal eq)

Binary

Hexadecimal

Octal

2) Laws \Rightarrow Moore law

\Rightarrow Commutative law

\Rightarrow duality \Rightarrow Associative

Theorem \Rightarrow distributive

\Rightarrow Demorgan

\Rightarrow Idempotent

\Rightarrow Law of complement

\Rightarrow Law of negation (inclusion)

\Rightarrow Law of absorption

\Rightarrow Consensus Law (on included factor law)

3) Forms of Boolean expression

\Rightarrow Minterms

\Rightarrow Maxterms

\Rightarrow SOP

\Rightarrow POS

4) Race condition

5) Eqn of HA, FA, HS, FS

6) Basic gates & universal gates

7) MUX & DEMUX

8) ENCODER & DECODER,
Priority encoder

9) K map, Quine Mc Cluskey

10) Flipflop & Latches \rightarrow storage element in dig. circuit

single bit storage (synchronous CKT)

edge triggering

SR FF $Q(n+1) = S + RQ(n)$

D FF $Q(n+1) = D$

JK FF $Q(n+1) = JQ'(n) + K'Q(n)$

T FF $Q(n+1) = T \oplus Q(n)$

Bi-stable multivibrator
2 stages

App of FF

\Rightarrow data storage

\Rightarrow transfer register

\Rightarrow Counter, register

\Rightarrow memory

\Rightarrow freq. division

Real time app of FF

\Rightarrow Counter display at bank

\Rightarrow token counters

\Rightarrow microwave oven timer

\Rightarrow fuel pump

\Rightarrow weighing machine

\Rightarrow vending machine

Because counter act only based on FF junction and it will count the value based on no. of FF used.

App of Encoder & decoder

\Rightarrow health monitoring machine

\Rightarrow RF based home automation system.

\Rightarrow Robotic vehicle with metal detector.

\Rightarrow used in communication syst.

like telecommunication

\Rightarrow networking, to transfer data

from one end to another

App of IC's

\Rightarrow computer

\Rightarrow microwave

\Rightarrow play station

\Rightarrow camera

\Rightarrow laptop

\Rightarrow memory device

\Rightarrow wrist watch

\Rightarrow TV, juicer maker

Priority encoder

It compresses multiple binary I/p's into a smaller no. of O/P. In encoder, no. of ~~I/p~~ I/p lines but only one of them get activated at time. In PE, more than one I/p get activated at same time.

App of shift reg

→ to store binary data
→ data transfer & manipulation

→ SISO → time delay to ckt.

→ convert serial data to

parallel data comm. lines.

&
parallel to serial.

SISO → used in communication (demultiplexing of data line)

PISO → convert parallel data to serial data (MUX)

PIPO → used as temporary storage

Bidirectional Shift reg → Shift by left ($\times 2$)
" " " " right ($\div 2$)

mode = 1 - right
0 - left

are the shift reg in which O/P are

connected back to I/P in order to

produce particular sequence.

Ring Counter Johnson Counters

→ It is basically a shift register counter in which the O/P of FF is connected to next FF and so on, and O/P of last FF is feedback into 1st FF.

→ It is self decoding, No extra decoding is needed to determine what state the counter is in.

→ data pattern with in shift reg will circulate as long as clock pulse are applied.

→ data pattern will repeat after every 4 clk pulses.

JOHNSON (TWISTED RING COUNTERS)

→ O/P of FF is connected to next FF and so on, but O/P of last FF is inverted and again feedback to 1st FF.

→ data pattern will repeat every 8 clk pulse.

Adv
it only need n no. of FF compared to ring counter to circulate a given data to generate sequence of 2n states.

COUNTERS

=> stores & displays the no. of times a particular event

(or) process has occurred.

=> Counting purpose

Asynchronous counter

Synchronous counter

(ripple counter)

(parallel clk)

-> In synchronous, has one global clk which drives each FF, so o/p changes parallelly.

=> Adv => does not have delay because same clk is given to each FF.

In asynchronous, we don't use universal clk, only first FF is driven by clk & clk I/P of rest of the following FF is driven by o/p of previous FF.

=> operate at high freq than asynchronous counter

up counter

down

up/down

mod counter ($2^n \geq N$)
counting seq

no. of FF used
no. of counter

Decade counter. (mod counter (or) BCD counter)

It counts ten different states & then over to its initial state. Will count from 0-9 (simple counter - also count 0 to 15) (for 4 bit counter).

App of counter

=> digital clk

=> freq counters

=> A to digital converter

=> design digital device by using counter

=> oven, washing machine and generator timer.

=> parity checker (even, odd)

=> Complements (to subtracting the numbers, Complements is used)

=> Conversion of FF

=> NAND / NOR Implementation

=> 3 state buffer

Conversion

BCD - (Normal)

Gray (EXOR)

Excess (+3)

ASCII

EXBIC

Error detecting code

Alpha numeric code

Binary -> Bcd.

Reducing method

⇒ K map (Karnaugh)

⇒ Tabulation method (Quin Mc Cluskey)

Memory — RAM

ROM — PROM, EPROM, EEPROM

Programmable Logic devices

PROM	AND array	OR array
PAL	fixed	programmable
PLA	programmable	fixed
	programmable	...

IC

Combinational

Sequential Clk

Analysis of synchronous seq clk

- ⇒ state eqn (or) characteristic eqn
- ⇒ state diagram
- ⇒ state table

state assignments

- ⇒ Binary code
- ⇒ Gray code
- ⇒ One hot assignment
- ⇒ universal register
- ⇒ serial adder

⇒ Mealy / Moore model

1) Combinational & sequential circuits

Combinational

⇒ O/P depends only on I/P.

⇒ Clk is not required.

⇒ Easy to design

⇒ faster in speed

⇒ memory not req

⇒ Eg: MUX, demux, encoder, decoder, adder, subtractor

Sequential

⇒ O/P depends on both present & past I/Ps.

⇒ Clk req

⇒ difficult

⇒ slower

⇒ memory req to store previous I/Ps.

Memory — FF — Sync clk

— Latch — Async clk

Eg: Register, Counter

Syn ckt

⇒ digital circuits are governed by clock signal.

⇒ O/P depends on I/P at discrete time.

⇒ Memory elements are used like clocked FF.

⇒ Time variable is discrete.

⇒ easy to design but low in operation.

⇒ No timing problem in feedback path.

⇒ Complex circuit, more expensive.

⇒ In these circuit, change in state occurs in response to clock pulse.

Eg: Counter, Shift reg, memory unit.

Asy ckt

digital circuits are not driven by clock signal. They are self-timed circuits.

O/P depends on sequence in which the I/P changes.

Memory elements are used like unlocked FF (or) time delay elements.

Time variable is continuous.

Difficult to design but faster in operation.

Problem involved in feedback path.

has few components, less expensive (economical).

In these circuits, state changes occur whenever I/P variable changes.

eg: Low power & high speed operation like simple microprocessors, digital signal processing units, in communication system for email application, internet access & networking.

Synchronous Counter

- ⇒ All FF are triggered with same clock simultaneously.
- ⇒ Faster in operation than any counter.
- ⇒ Does not produce any decoding errors.
- ⇒ Also called as parallel counter.
- ⇒ Designing & implementation are complex due to increasing no. of states.
- ⇒ will operate in any desired count sequence.
- ⇒ Eg: ring, Johnson counter.
- ⇒ propagation delay is less.

Asynchronous Counter

- ⇒ different FF are triggered with different clock not simultaneously.
- ⇒ Slower.
- ⇒ produce decoding error.
- ⇒ serial counter.
- ⇒ Very easy.
- ⇒ will operate only in fixed count sequence (up/down).
- ⇒ Eg: Ripple up counter, ripple down.
- ⇒ High propagation delay.